

EE344:ELECTRONIC DESIGN LAB  
SOLAR POWERED STREET  
LIGHT: BATTERY MANAGEMENT  
SYSTEM

Group 12

Adway Girish (180070002)

Saksham Gupta (180070049)

Samar Jain (180010052)

Faculty Mentor: Prof. Joseph John

Project Objective: To prolong the lifetime of batteries used in solar powered street lights by maintaining their voltage within optimal limits

# DESIGN APPROACH

The four subsystems and their primary objectives are

1. Overvoltage Protection: Ensuring that the voltage across the battery is limited to 14.7 V
2. Undervoltage Protection: Stopping discharge when the voltage reaches 10.5 V
3. Load Control Circuit: Automatically turn the LED on when its sufficiently dark
4. State of Charge Measurement: Measure and display the SoC on an LCD screen

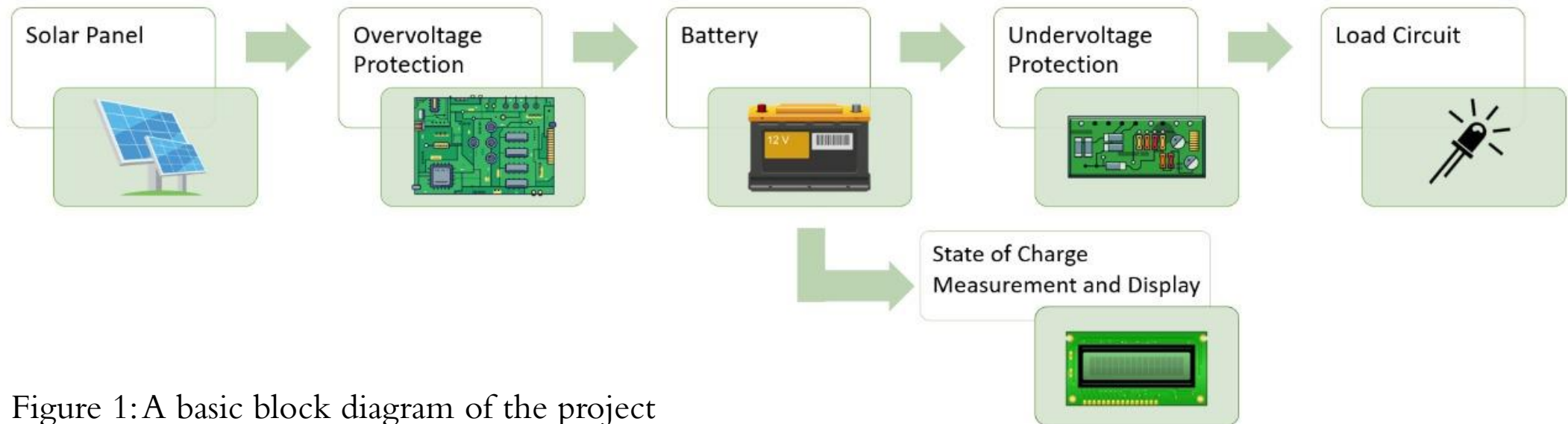


Figure 1: A basic block diagram of the project

# OVERVOLTAGE PROTECTION CIRCUIT

The key aspects of this subsystem are as follows:

1. LM317 used as adjustable voltage regulator to generate 14.7 V
2. LM324 used to compare the battery voltage to LM317 output
3. LM324 energizes the relay and disconnects battery when supply voltage exceeds 14.7 V

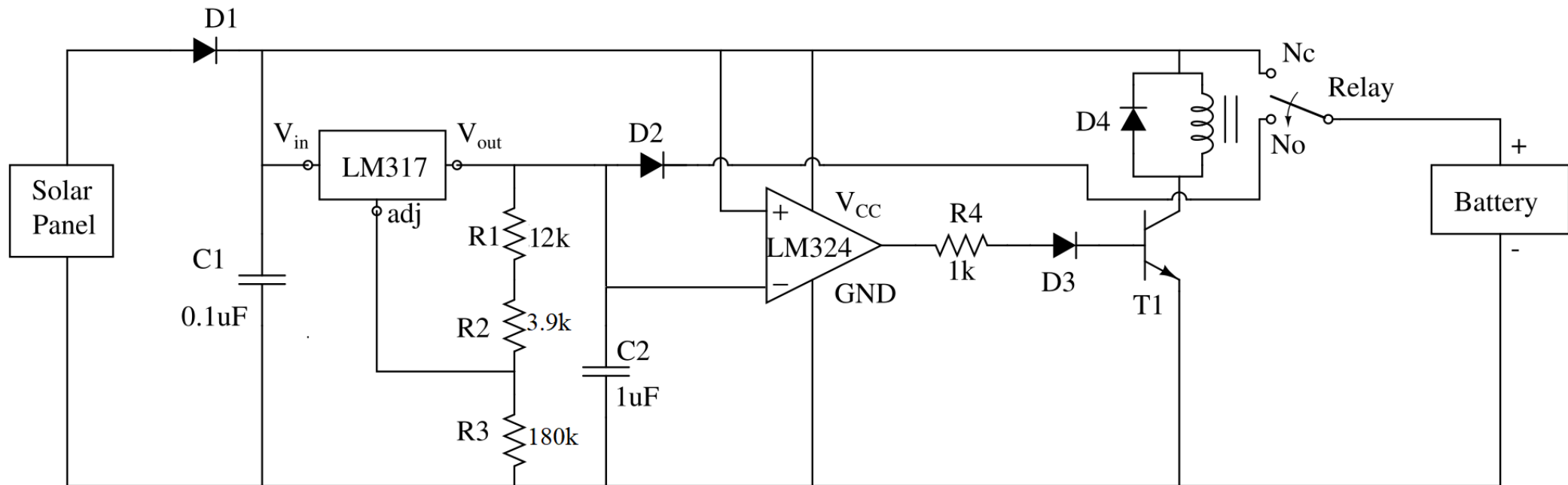


Figure 2: Overvoltage Protection Circuit

# UNDERVOLTAGE PROTECTION CIRCUIT

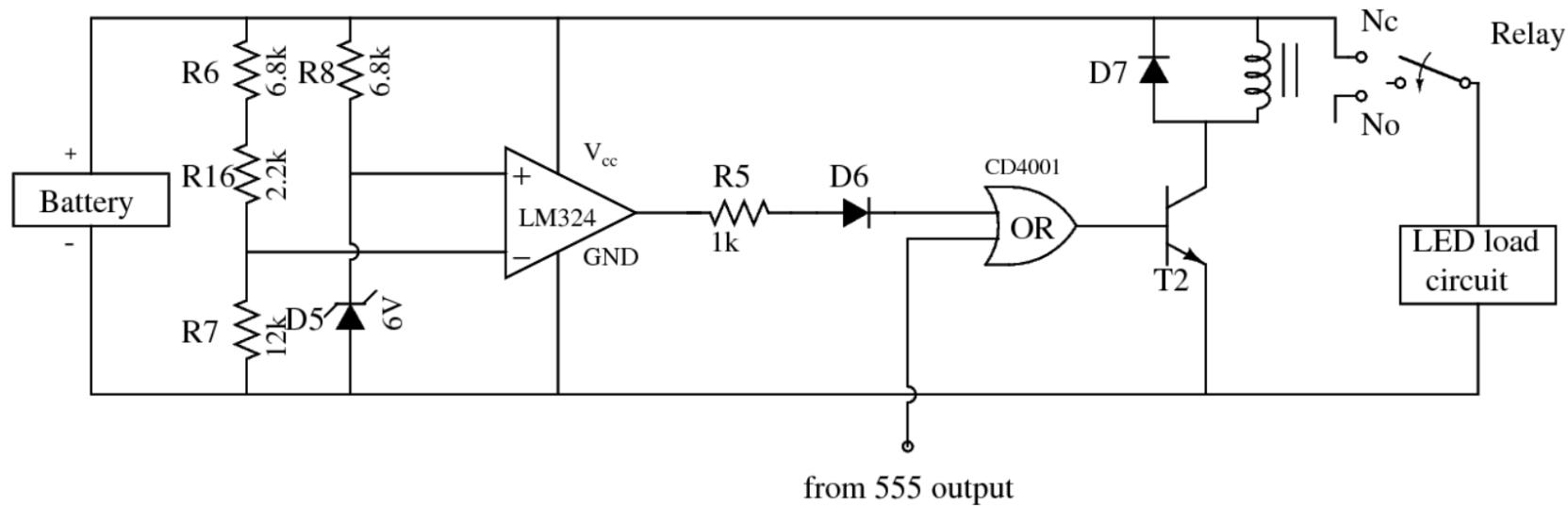


Figure 3: Undervoltage Protection Circuit

# LOAD CONTROL CIRCUIT

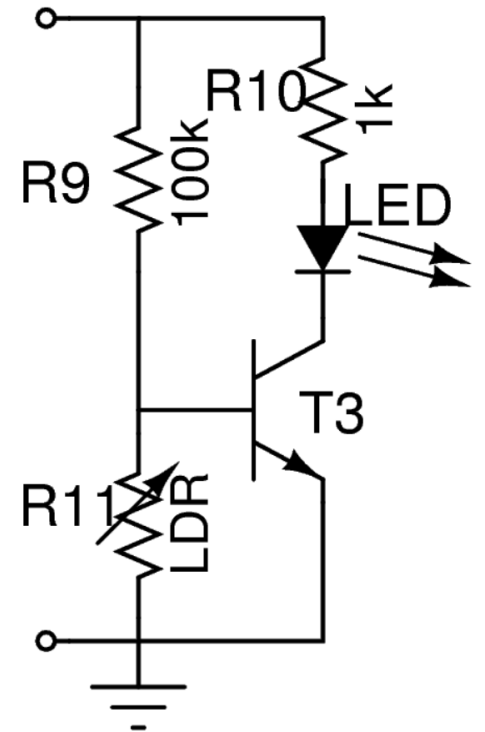


Figure 4: Load Control Circuit

# STATE OF CHARGE MEASUREMENT

The key aspects of this subsystem are as follows:

1. LM555 timer in monostable vibrator mode disconnects the LED load for 5 minutes to power Pt-51 and ADC
2. Battery voltage is converted to a digital input and fed into the microcontroller which calculates SoC

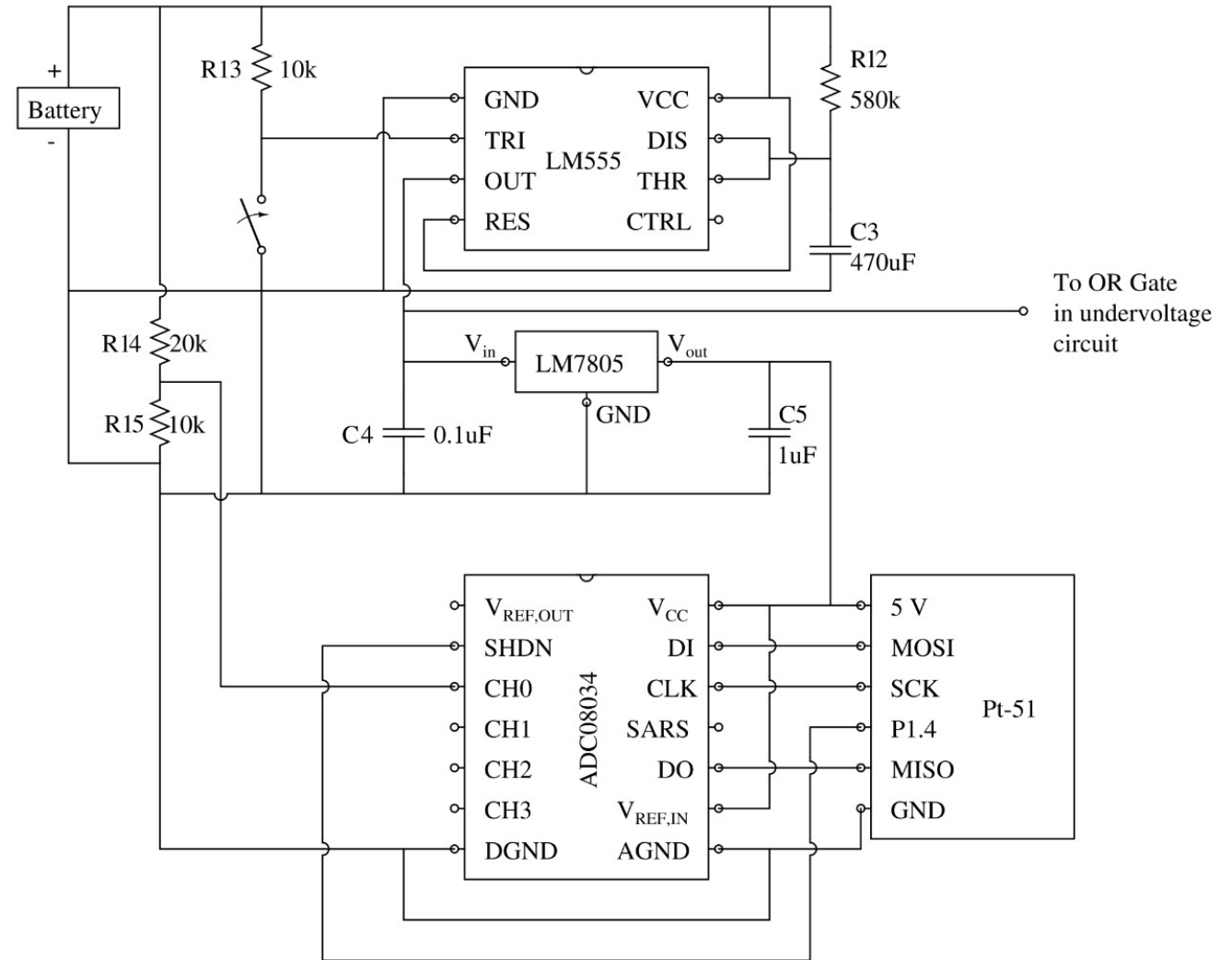


Figure 5: SoC Measurement and Display Circuit

THANK YOU

# BACKUP 1: PCB DESIGN

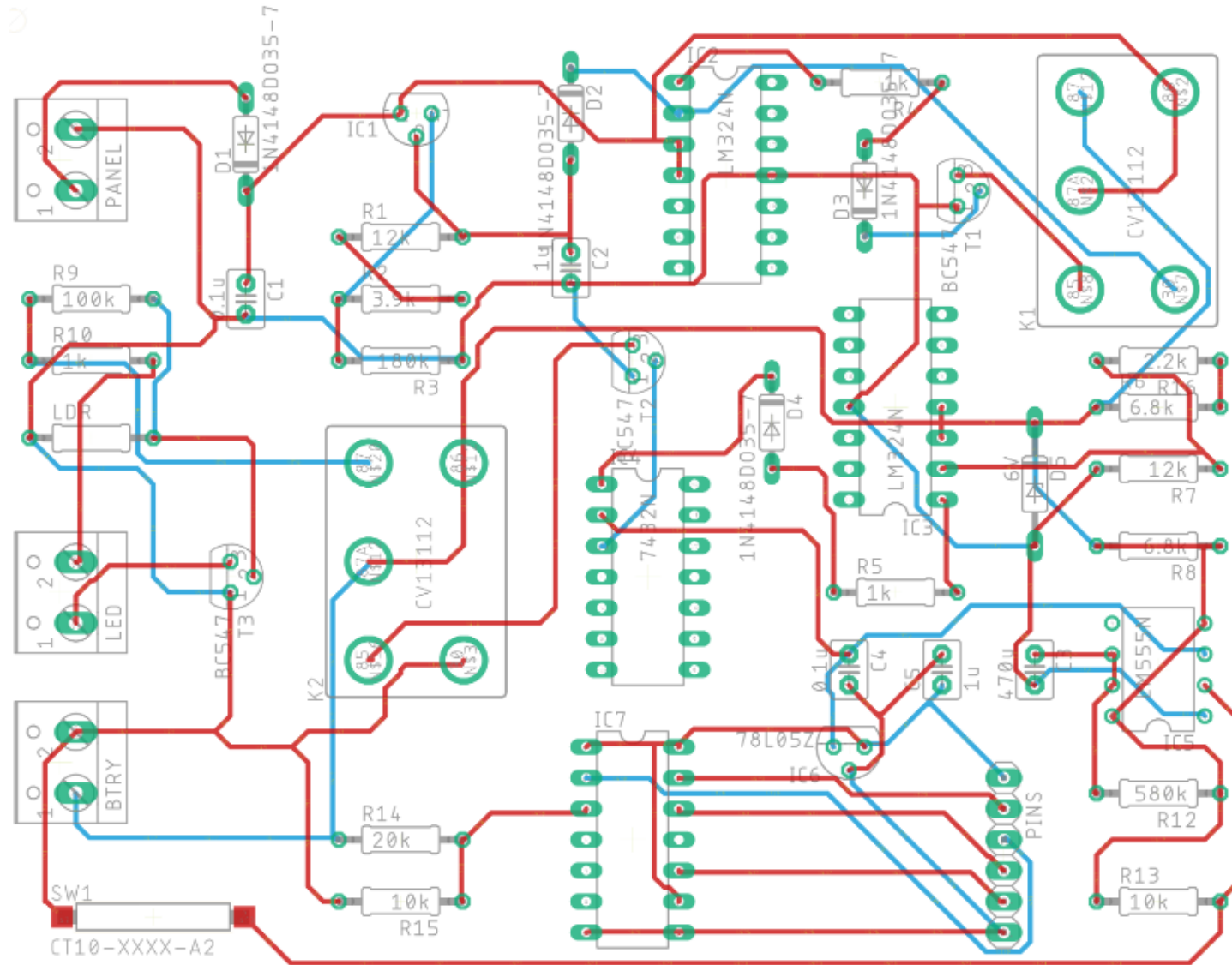


Figure 6: PCB designed

# BACKUP 2: BILL OF MATERIALS

Qty	Value/Device	Parts	Description	Cost per Qty (in Rs.)
1	ADC08034N	IC7	A/D Converter	350
1	LM317L	IC1	Voltage Regulator	50
1	PINHD-1X6	PINS	Pin header	5
3	W237-102	BTRY, LED, PANEL	WAGO Screw clamp	15
2	0.1u	C1, C4	Capacitor	10
2	1u	C2, C5	Capacitor	10
1	470u	C3	Capacitor	50
1	100k	R9	Resistor	2
2	10k	R13, R15	Resistor	2
2	12k	R1, R7	Resistor	2
1	180k	R3	Resistor	3
3	1k	R4, R5, R10	Resistor	2
1	2.2k	R16	Resistor	2
1	20k	R14	Resistor	2
1	3.9k	R2	Resistor	2
1	580k	R12	Resistor	2
2	6.8k	R6, R8	Resistor	2
4	1N4148	D1, D2, D3, D4	Diode	10
1	6V	D5	6 volt Zener Diode	10
1	7432N	IC4	Quad 2-input OR gate	20
1	78L05Z	IC6	Positive Voltage Regulator	10
3	BC547	T1, T2, T3	NPN Transistor	10
1	CT10-XXXX-A2	SW1	CT10 Series Molded Switch	50
2	CV13112	K1, K2	Micro-280 Relay	150
1	LDR	R11	Light dependent resistor	100
2	LM324N	IC2, IC3	Single supply opamp	100
1	LM555N	IC5	Timer	10
Total (on PCB) :				1,341
1	Pt-51 kit		8051 Microcontroller	500
1	10W, 18V		Solar panel	500
1	5W		LED load	50
1	12V		UP-PW1245P Battery	1500
1	16x2 with HD44780		LCD screen	100
Total :				3,991